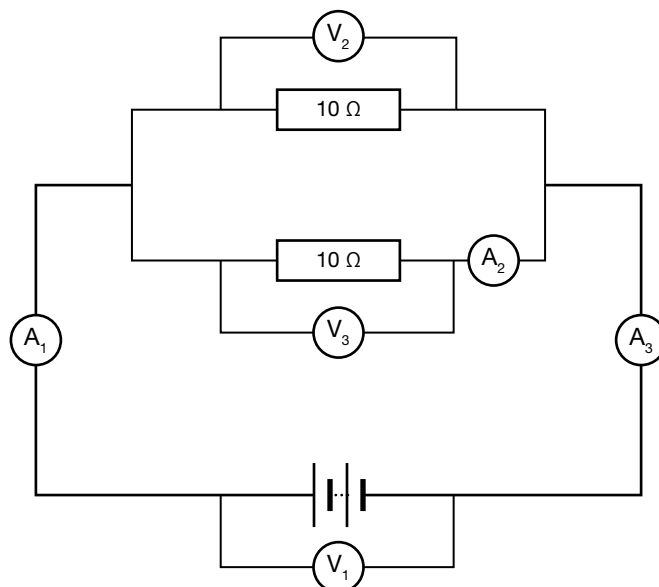


# Current, resistance and potential difference and resistors

In the following circuit  $V_1 = 5\text{V}$  and  $A_1 = 1\text{A}$ . Complete the missing values. (2 marks, ★★★)



$A_2 =$  .....

$A_3 =$  .....

$V_2 =$  .....

$V_3 =$  .....

## NAILIT!

Knowing the  $I$ - $V$  characteristics for the following components is essential: wire, resistor, filament lamp and diode.

Make sure that you know how to get the data from an experiment and then how you would plot a graph of  $I$ - $V$  to observe whether the component always follows Ohm's law.

Which of those 4 components are ohmic and which are non-ohmic?

## DO IT!

Practise sketching the  $I$ - $V$  graph for a component that follows Ohm's law. Annotate how you would work out the resistance of the component if the graph is a straight line.

Remember that if you put potential difference on the  $x$ -axis and current on the  $y$ -axis, then the gradient will not be the resistance.

It is  $\frac{1}{\text{resistance}}$