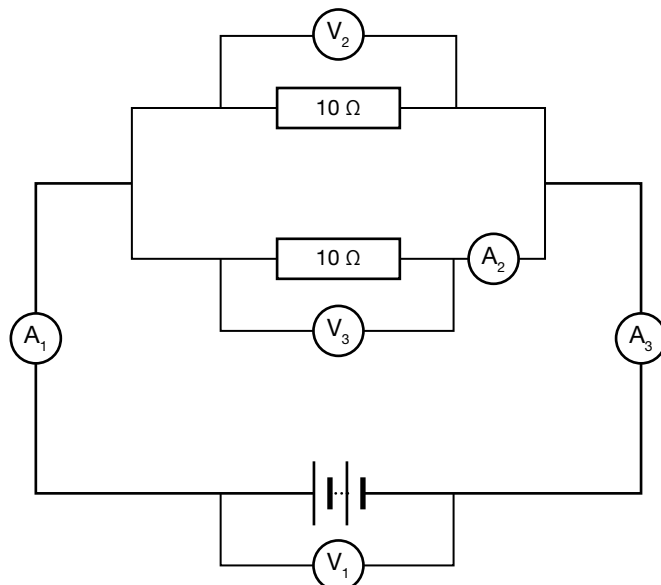


Current, resistance and potential difference and resistors

In the following circuit $V_1 = 5\text{ V}$ and $A_1 = 1\text{ A}$. Complete the missing values. (2 marks, ★★★)



$A_2 = \dots\dots\dots$ $A_3 = \dots\dots\dots$ $V_2 = \dots\dots\dots$ $V_3 = \dots\dots\dots$




NAILIT!

Knowing the I - V characteristics for the following components is essential: wire, resistor, filament lamp and diode.

Make sure that you know how to get the data from an experiment and then how you would plot a graph of I - V to observe whether the component always follows Ohm's law.

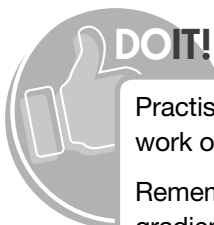Which of those four components are ohmic and which are non-ohmic?



Practise sketching the I - V graph for a component that follows Ohm's law. Annotate how you would work out the resistance of the component if the graph is a straight line.

Remember that if you put potential difference on the x -axis and current on the y -axis, then the gradient will not be the resistance.

It will be the reciprocal of the resistance or $\frac{1}{\text{resistance}}$.