

Electricity Makes Things Work

Name: _____

Draw an **open** circuit.



The light is _____

because _____

Draw a **closed** circuit.

The light is _____


because _____

Electricity can be made by:

Electricity Makes Things Work

Name: _____

Electricity flows in a **circuit**.

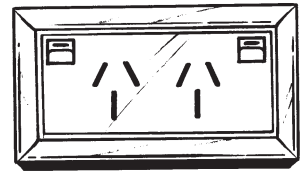

This is an **open circuit** because _____

This is a **closed circuit** because _____

The electrical circuit in a toaster is **open** when

The electrical circuit in a toaster is **closed** when
